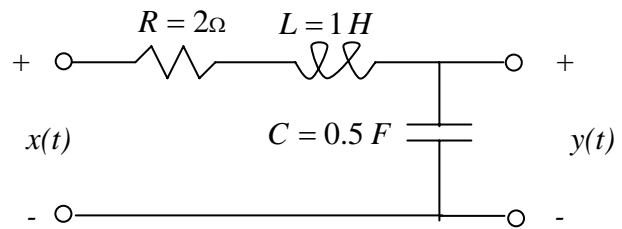


Assignment #08

ECSE-2410 Signals & Systems - Spring 2011

Due Tue 02/22/11

1(80). Consider the RLC circuit shown,



- (a)(5). Find $H(s)$.
- (b)(5). Find the input-output differential equation for this circuit.
- (c)(10). Use Simulink to implement the differential equation with summer and integrator blocks (no overall single large transfer function). Use format pull-down menu to figure out how to flip a block so that the input is on the right and the output is on the left.
- (d)(5). Is the system overdamped, critically damped, underdamped or undamped? Justify your answer. Sketch the pole-zero plot.
- (e)(10). Find the impulse response, $h(t)$.
- (f)(10). Use Matlab to plot the impulse response equation you found in (e).
- (g)(10). Use the Matlab command `impz(num,den)` to plot the system impulse response and compare this plot to the one in (f). Do a 'help impz' for more information.
- (h)(10). Find the analytical equation for the system **step** response.
- (i)(10). Use the Matlab symbolic toolbox to find the equation for the system step response. Compare this to your result in (h).
- (j)(5). Use the Matlab command `step(num,den)` to plot the system step response. Do a 'help step' for more details.

2(20). The following pole-zero diagrams represent the transfer function, $H(s)$ of four *different* systems. For *each case* find the

- (a)(4) damping factor, ζ (b)(4) natural frequency, ω_n (c)(4) damped frequency, $\omega_d = \omega_n \sqrt{1 - \zeta^2}$,

and answer the questions: for which system

(d)(4) (A,B,C,or D?) does the step response have the fastest rate of decay?

(e)(4) (A,B,C,or D?) does the step response have the highest damped frequency of oscillation?

